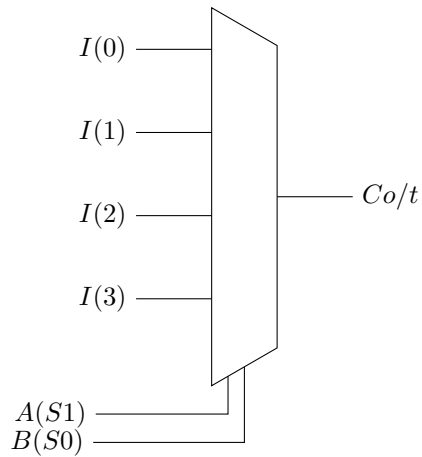


Assignment 9 (GATE, EC2018,18)

SIKANDER KATHAT

15 December 2020

1 Question 18 MUX diagram



2 Question 18

A 4:1 multiplexer is to be used for generating the output carry of a full adder. A and B are the bits to be added while $C(in)$ is the input carry and Co/t is the output carry. A and B are to be used as select bits with A being more significant select bit.

Which one of the following statement correctly describes the choice of signals to be connected to the inputs $I(0)$, $I(1)$, $I(2)$ and $I(3)$ so that the output is Co/t ?

1. $I(0) = 0, I(1) = C(in), I(2) = C(in), I(3) = 1$
2. $I(0) = 1, I(1) = C(in), I(2) = C(in), I(3) = 1$
3. $I(0) = C(in), I(1) = 0, I(2) = 1, I(3) = C(in)$
4. $I(0) = 0, I(1) = C(in), I(2) = 1, I(3) = C(in)$

3 Solution

TRUTH TABLE-

A	B	C(in)	Sum(S)	Co/t
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Kamp for Sum(S)-

		$BC(in)$			
		00	01	11	10
A	0	0	1	0	1
	1	1	0	1	0

Boolean expression for Sum(S)-

$$S = \overline{A} \overline{B} \overline{C(in)} + \overline{A} \overline{B} C(in) + \overline{A} B \overline{C(in)} + A B C(in)$$

Kmap for Co/t-

		$BC(in)$			
		00	01	11	10
A	0	0	0	1	0
	1	0	1	1	1

Boolean expression for Co/t-

$$Co/t = BC(in) + AB + AC(in)$$

A	B	C o/t
0	0	0
0	1	C(in)
1	0	C(in)
1	1	1

TRUTH TABLE FOR Co/t to be output-

//

So, by the truth table for Co/t to be output, we get
 $I(0)=0$, $I(1)= C(in)$, $I(2)= C(in)$ and $I(3)= 1$