

Assignment 9 (GATE, EC2018,18)

SIKANDER KATHAT

25 December 2020

1 Question 18 MUX diagram

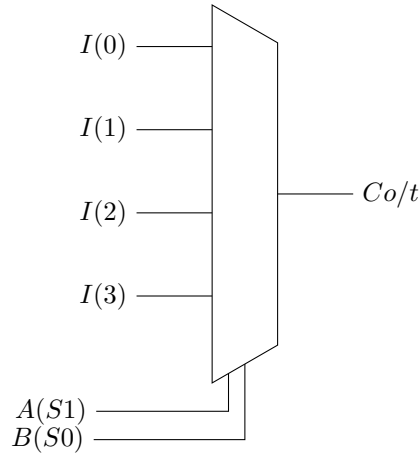


Figure 1: question MUX diagram

2 Question 18

A 4:1 multiplexer is to be used for generating the output carry of a full adder. A and B are the bits to be added while C(in) is the input carry and Co/t is the output carry. A and B are to be used as select bits with A being more significant select bit.

Which one of the following statement correctly describes the choice of signals to be connected to the inputs I(0), I(1), I(2) and I(3) so that the output is Co/t?

1. $I(0) = 0, I(1) = C(in), I(2) = C(in), I(3) = 1$
2. $I(0) = 1, I(1) = C(in), I(2) = C(in), I(3) = 1$

3. $I(0) = C(in), I(1) = 0, I(2) = 1, I(3) = C(in)$
4. $I(0) = 0, I(1) = C(in), I(2) = 1, I(3) = C(in)$

3 Solution

A	B	C(in)	Sum(S)	Co/t
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Table 1: TRUTH TABLE

		$BC(in)$			
		00	01	11	10
A	0	0	1	0	1
	1	1	0	1	0

Figure 2: k-map for Sum(S)

Boolean expression for Sum(S)-
 $S = \overline{A} \overline{B} \overline{C(in)} + \overline{A} \overline{B} C(in) + \overline{A} B \overline{C(in)} + ABC(in)$

		$BC(in)$			
		00	01	11	10
A	0	0	0	1	0
	1	0	1	1	1

Figure 3: k-map for Co/t

Boolean expression for Co/t-
 $Co/t = BC(in) + AB + AC(in)$

A	B	C o/t
0	0	0
0	1	C(in)
1	0	C(in)
1	1	1

Table 2: TRUTH TABLE for Co/t to be output

So, by the truth table for Co/t to be output, we get
 $I(0)=0$, $I(1)= C(in)$, $I(2)= C(in)$ and $I(3)= 1$